Lesson 12 Analog Joystick Module

Introduction

In this lesson, you will learn how to use the analog joystick module to add some control in your projects.

Hardware Required

- ✓ 1 * RexQualis UNO R3
- ✓ 1 * Breadboard
- ✓ 1 * Joystick module
- ✓ 5 * F-M Jumper Wire

Principle

Analog Joystick Module

The module has 5 pins: VCC, Ground, X, Y, Key. Note that the labels on yours may be slightly different, depending on where you got the module from. The thumb stick is analog and should provide more accurate readings than simple 'directional'



joysticks tact use some forms of buttons, or mechanical switches. Additionally, you can press the joystick down (rather hard on mine) to activate a 'press to select' push-button.

We have to use analog Arduino pins to read the data from the X/Y pins, and a digital pin to read the button. The Key pin is connected to ground, when the joystick is pressed down, and is floating otherwise. To get stable readings from the Key /Select pin, it needs to be connected to VCC via a pull-up resistor. The built in resistors on the Arduino digital pins can be used. For a tutorial on how

to activate the pull-up resistors for Arduino pins, configured as inputs.

We need 5 connections to the joystick. The connections are: Key, Y, X, Voltage ,and Ground. "Y and X" are Analog and "Key" is Digital. If you don' t need the switch then you can use only 4 pins.

Code interpretation

//74HC595 pin 9 STCP

```
const int SW_pin = 3; // input for detecting whether the
jotstick/button is pressed
```

const int X_pin = A0; // analog pin connected to X output

const int Y_pin = A1; // analog pin connected to Y output

void setup() {

pinMode(SW_pin, INPUT);	//setup SW input
digitalWrite(SW_pin, HIGH);	//reading button state:1=not
pressed,0=pressed	

```
Serial.begin(9600); //Seput serical connection for
```

print out to console

```
} //print out values
```

void loop() {

Serial.print("Switch: ");

Serial.print(digitalRead(SW_pin));

Serial.print("\n");

Serial.print("X-axis: ");

Serial.print(analogRead(X_pin));

```
Serial.print("\n");
Serial.print("Y-axis: ");
Serial.println(analogRead(Y_pin));
Serial.print("\n\n");
delay(2000);
```

Experimental Procedures

Step 1:Build the circuit

}

We need 5 connections to the joystick.

The connections are: K, Y, X, Voltage and Ground.

"Y and X" are Analog and "K" is Digital. If you only need Any one switch then you can use only 3 pins.



Schematic Diagram



Step 2: Open the code:Analog_Joystick_Code

Blinking_LED_C	Code Arduino 1	L.8.5			
File Edit Sketch	Tools Help				
oo de				Ø	
🕌 Open an Arc	luino sketch				×
查找范围(I):	🔒 Analog_Joy	stick_Code	- 0	🌶 📂 🛄 🗸	
Ca	名称	^		修改日期	i.
最近访问的位置	💿 Analog_Jo	ystick_Code.ino		2017/11/6 14	4:37 /
桌面					
库					
计算机					
	1	m			
网络		10 GD04 10 -	· · · · · ·	<u> </u>	1777 (2)
	对象名称(U):	AC-SKU4_UItrasoni	_Sensor_Module_	Lode V	£1#@
	对象类型(I):	All Files (*.*)			取消
			1		ai
GIODAL VARIADIES	use a bytes (0%) of dynamic memory,	Teaving 2024 P	vies for f	
•	Ш			F	
Arduino/Genuino Uno on COM118					

Step 3: Attach Arduino UNO R3 board to your computer via USB cable and check that the 'Board Type' and 'Serial Port' are set correctly.

Step 4: Upload the code to the RexQualis UNO R3 board.

Step 5: Open the Serial Monitor then you can see the data as below:

(How to use the Serial Monitor is introduced in details in Lesson 0 Preface)

💿 COM12 (Arduino/Genuino Uno)	
	Send
X-axis: 249	*
Y-axis: 0	
Switch: 1	
X-axis: 276	
I-axis: U	
Switch: 1	
X-axis: 1022	
Y-axis: 1022	
Switch: 1	
X-axis: O	
Y-axis: 503	
Switch: 0	
X-axis: 521	
Y-axis: 503	
Switch: 1	
X-axis: 521	
Y-axis: 503	=
	-
Autoscroll	[No line ending \checkmark] [9600 baud \checkmark]

Then, Turn the joystick so you can see the data changes on the monitor.



If it isn' t working, make sure you have assembled the circuit correctly, verified and uploaded the code to your board. For how to upload the code and install the library, check Lesson 0 Preface.